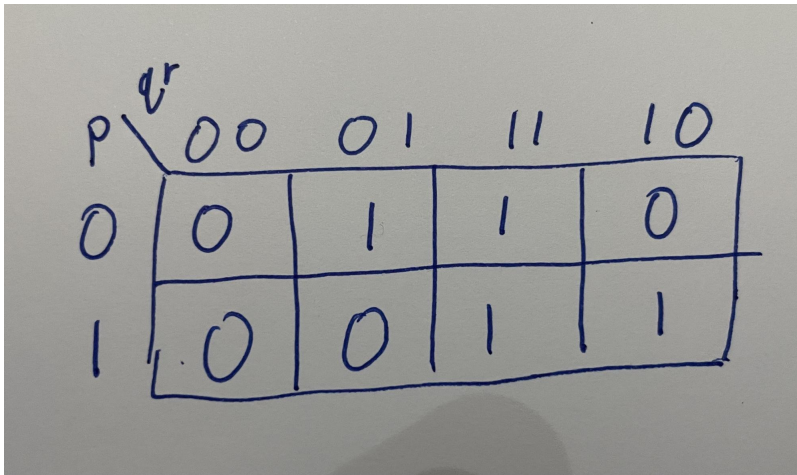


ECE M16 Homework 2

Lawrence Liu

July 13, 2022

HW1 Problem 4 part b



A handwritten truth table for a 2-input function. The inputs are labeled p and q . The outputs are labeled 0 and 1. The table is a 2x4 grid with columns for q (00, 01, 11, 10) and rows for p (0, 1). The values in the cells are: (0, 00) = 0, (0, 01) = 1, (0, 11) = 1, (0, 10) = 0; (1, 00) = 0, (1, 01) = 0, (1, 11) = 1, (1, 10) = 1.

$p \backslash q$	00	01	11	10
0	0	1	1	0
1	0	0	1	1

HW1

Problem 7

(a)

Month	m3	m2	m1	m0	output
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1


(b)

m1 \ m0	00	01	10	11
00	1	0	0	0
01	1	1	0	0
10	0	1	0	1
11	0	0	1	1

Therefore the equation is:

$$m_0 \cdot \overline{m_3} + \overline{m_0} \cdot m_3$$


(c)

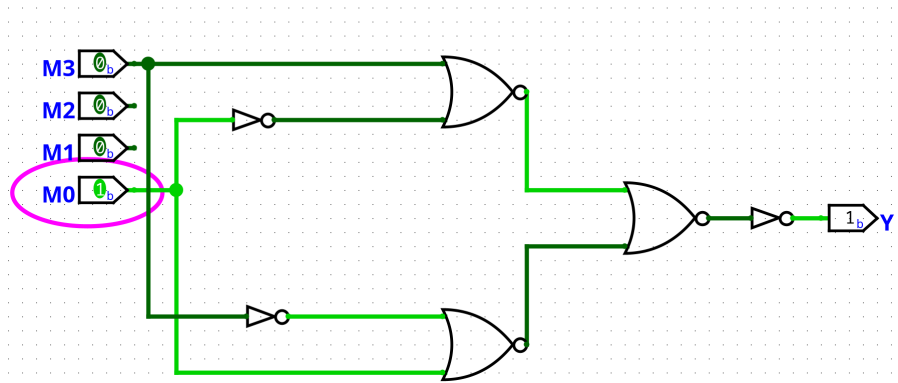

HW 2

Problem 1

There would be a static 0 hazard between $b = 1, c = 1, a = 0$ and $b = 1, c = 1, a = 1$. We can fix it with the following circuit. We can fix this by adding an And gate between b and c before the nor, so the resulting function would look like this

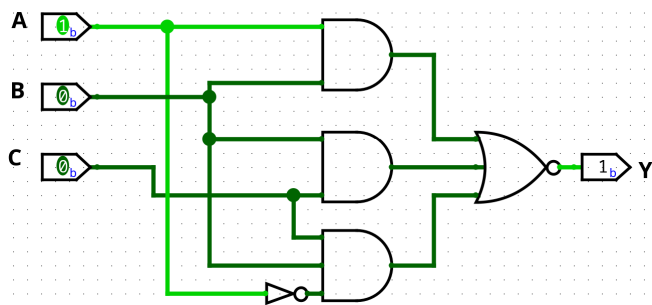

Problem 2

Let the inputs be $M[0 : 3]$ then we have the following truth table

decimal	M3	M2	M1	M0	q2	q5
0	0	0	0	0	1	1
1	0	0	0	1	0	1
2	0	0	1	0	1	1
3	0	0	1	1	0	1
4	0	1	0	0	0	1
5	0	1	0	1	0	0
6	0	1	1	0	1	0
7	0	1	1	1	0	1
8	1	0	0	0	1	1
9	1	0	0	1	0	1

Therefore we will have the following Kmap for q2

		$q2$ $M1, M0$			
		00	01	11	10
$M3, M2$	00	1	0	0	1
	01	0	0	0	1
	11	-	-	-	-
	10	1	0	-	-

Therefore the equation for q2 is:

$$q2 = \overline{M2} \cdot \overline{M0} + M1 \cdot \overline{M0}$$


Likewise, the Kmap for q5 is

		$q5$ $M1, M0$			
		00	01	11	10
$M3, M2$	00	1	1	1	1
	01	1	0	1	0
	11	-	-	-	-
	10	1	1	-	-

Therefore the equation for q5 is:

$$q5 = \overline{M2} + \overline{M1} \cdot \overline{M0} + M1 \cdot M0$$

Therefore the resulting circuit is

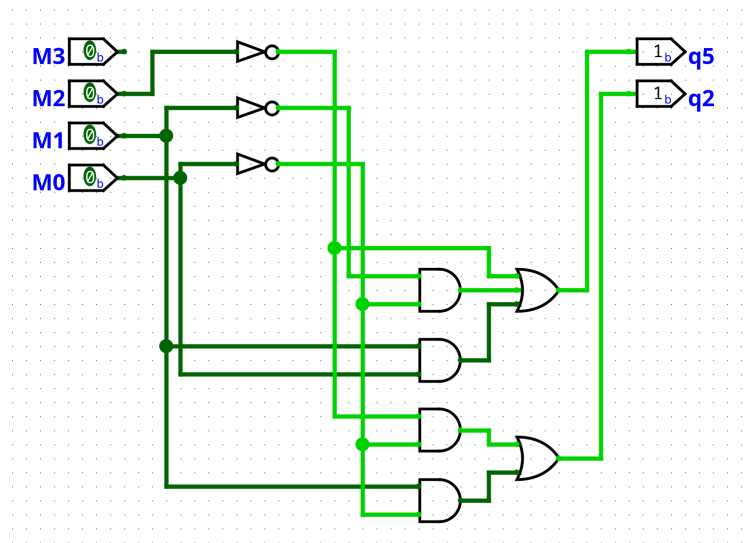

Problem 3

