

ECE M16 Homework 2

Lawrence Liu

July 29, 2022

Problem 1

(a)

It will toggle, if the latch is reset, ie $Q = 0$ and $\bar{Q} = 1$. Then the output will be $Q = 1$ and $\bar{Q} = 0$ following the clock pulse

(b)

if $C = 0$ it will latch, but with $C = 1$ there will be following transition table

J	K	Q current	Q next
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Therefore this is like a SR latch however it will toggle at $J = K = 1$, unlike the SR latch.

(c)

		$J^n K^n$			
		00	01	11	10
Q^n	0	0	0	1	1
	1	1	0	0	1

$$Q^{n+1} = J^n \cdot \overline{Q^n} + \overline{K^n} \cdot Q^n$$

(d)

The transition table of the D latch is:

C	D	Q next
0	x	Q
1	0	0
1	1	1

Which is the same as the transition table of the JK latch with $J = \bar{K} = D$.

C	J=D	$K = \bar{D}$	Q next
0	x	x	Q
1	0	1	0
1	1	0	1

Problem 3

(a)

The kmaps for assignment 1 are:

y_1


$x \backslash (y_1, y_0)^n$	00	01	11	10
0	0	0	0	1
1	0	1	1	1

and


y_0

$x \backslash (y_1, y_0)^n$	00	01	11	10
0	0	0	0	0
1	1	0	0	0

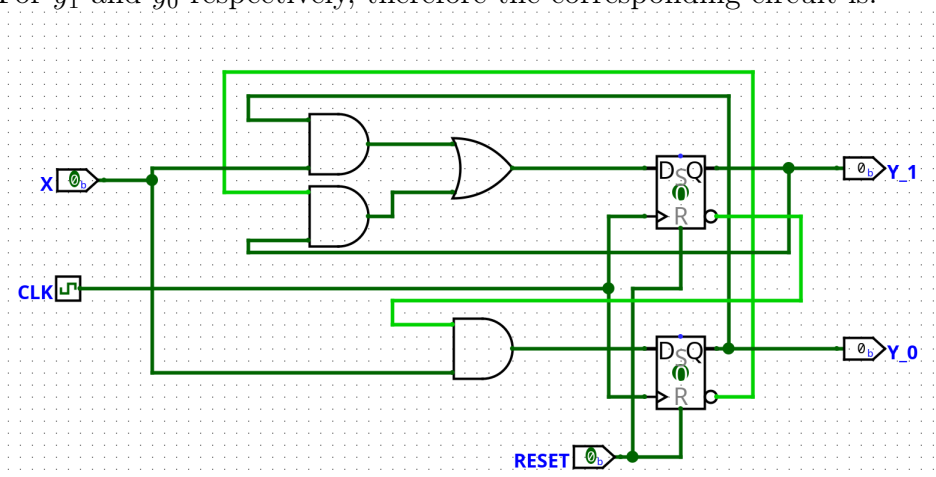
For y_1 and y_0 respectively, therefore the corresponding circuit is:



 
Likewise for assignment 2, the kmaps are:



and

 

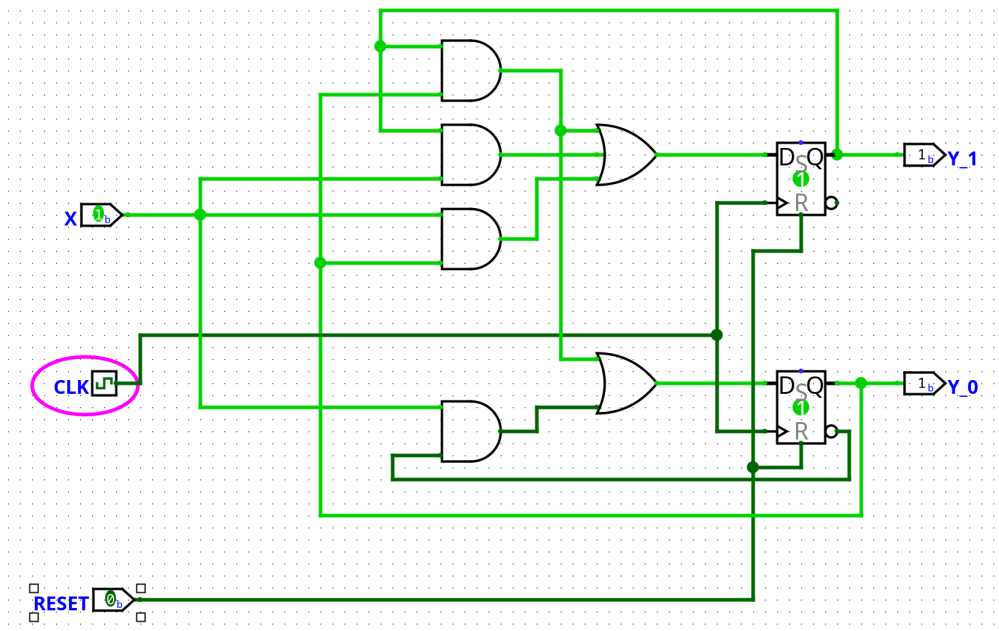For y_1 and y_0 respectively, therefore the corresponding circuit is:




(b)


Therefore assignment 1 is more economical since it uses less gates.

 Problem 4

Because we can use D flip flops to delay a signal, we have the following circuit




With the following timing diagram

 


 Problem 5

Once again we can use D flip flops to delay the signal, therefore using a mux we have the following circuit



With the following timing diagram

 

Problem 6


Let the remainder at step n be r_n , if the input bit is 0 we get that the remainder at step $n + 1$ is

$$r_{n+1} = (2r_n) \% 6$$

and if the input bit is 1 we get that the remainder at step $n + 1$ is

$$r_{n+1} = (2r_n + 1) \% 6$$

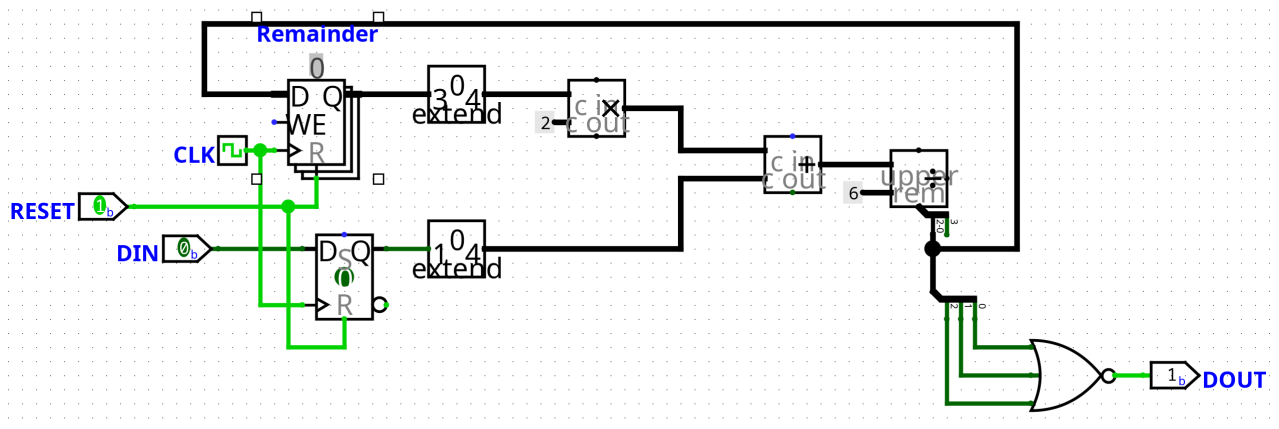. Therefore we have the following circuit



With the following timing diagram

