

# ECE M16 Final

Lawrence Liu

August 11, 2022

## Problem 1

	1	1	0	1
1	11	00	00	10
	1			
101	10	00		
	1	01		
1100	11	00		
	0			
	11	00	10	
11001	1	10	01	
	1	10	01	


## Problem 2

Basing on the assumption that  $c[1 : 0] = 11$  corresponds with  $o[1 : 0] = i[1 : 0]$  we have that

$$\begin{aligned} a[1] &= \overline{c[1]}. \overline{c[0]}. i[7] + \overline{c[1]}. c[0]. i[5] + c[1]. \overline{c[0]}. i[3] + c[1]. c[0]. i[1] \\ &= \overline{c[1]}. (\overline{c[0]}. i[7] + c[0]. i[5]) + c[1]. (\overline{c[0]}. i[3] + c[0]. i[1]) \end{aligned}$$

$$\begin{aligned} a[0] &= \overline{c[1]}. \overline{c[0]}. i[6] + \overline{c[1]}. c[0]. i[4] + c[1]. \overline{c[0]}. i[2] + c[1]. c[0]. i[0] \\ &= \overline{c[1]}. (\overline{c[0]}. i[6] + c[0]. i[4]) + c[1]. (\overline{c[0]}. i[2] + c[0]. i[0]) \end{aligned}$$

Which results in a circuit like this

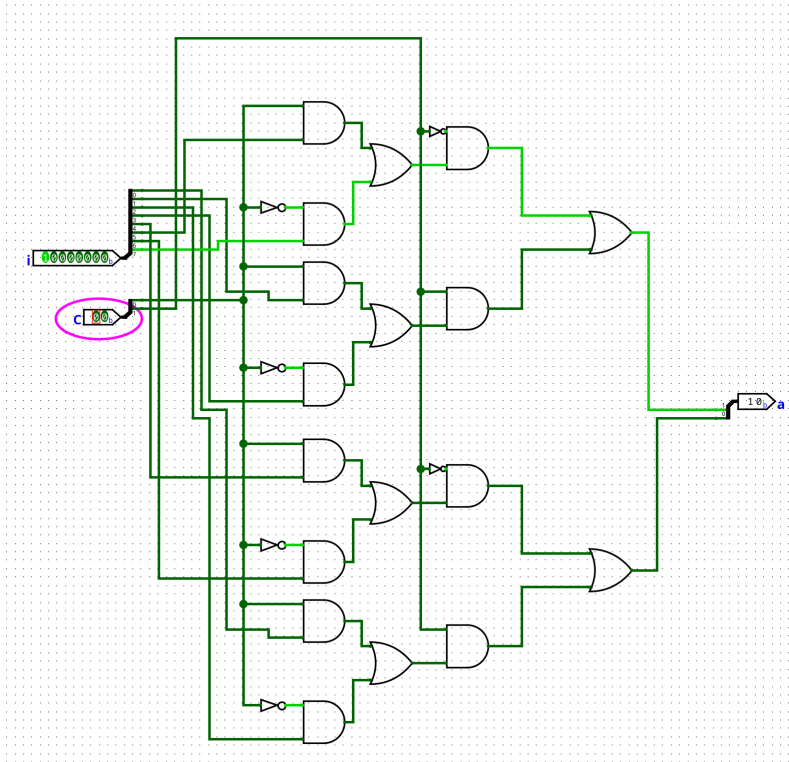

## Problem 3

I created the circuit, and it is shown above, and I tested it with the following python checker script

```

1 import numpy as np
2 import pandas as pd
3 import os
4 from calendar import monthrange
5
6 def RunCircuit(logisim_jar : str, circuit : str):
7     """
8     This function runs the logisim simulator and returns the output of
9     the circuit as
10    a pandas dataframe.
11    """
12    output=os.popen(f"java -jar {logisim_jar} {circuit} -tty table").
13    read()
14    output=[o.split() for o in output.split("\n")[:-1]]
15    return pd.DataFrame(output[1:], columns=output[0])
16
17 def checkQ2(truth_table:pd.DataFrame)->bool:
18     """
19     This function checks the output of the circuit for the truth table
20     and returns
21     weather the output is correct or not.

```

```

19     """
20     #convert hex to binary
21     truth_table['i']=truth_table['i'].apply(lambda x: f'{int(x,16):0>8b}
22     ')
23     for i,row in truth_table.iterrows():
24         c=int(row.C,2)
25         i=row.i
26         a=row.a
27         #calculate a expected
28         a_expected=i[c*2:c*2+2]
29         #check if a is equal to a_expected
30         if a!=a_expected:
31             print("error!")
32             print(f"at c={row.C}")
33             print(f"expected a={a_expected}")
34             print(f"got a={a}")
35             print(f"i={row.i}")
36             return False
37         return True
38
39 if __name__=="__main__":
40     truth_table=RunCircuit("../logisim-evolution.jar","logisim/FinalQ3.
41     circ")
42     if checkQ2(truth_table):
43         print("Q2 passed!")

```

This script utilizes Logisim's command line ability. I had the files in the following format

ECEM16


```

|- .gitignore
|- Final
| |-logisim
| | |- FinalQ3.circ
| :
| :
| |- checker.py
|- .gitignore
|- logisim-evolution.jar


```
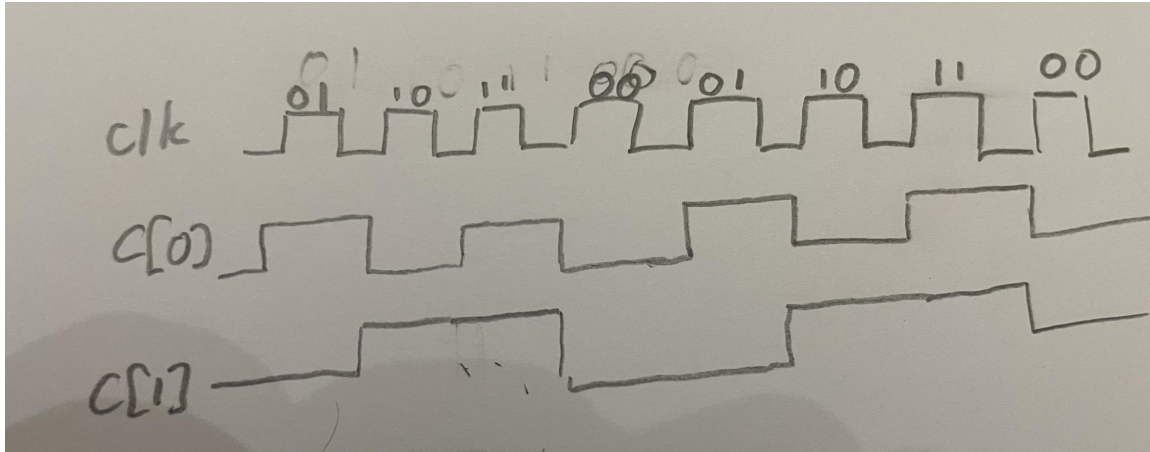
## Problem 4


Let  $c[1 : 0]$  be the desired output from our counter: we want the following timing diagram:



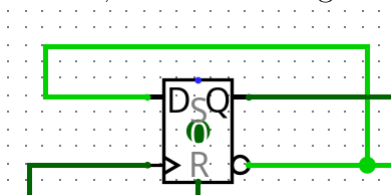
The first thing we notice is that  $c[0]$  is just the clock input but with a period twice of clock, and  $c[1]$  is just the clock input with a period of 4 times clock. We can make the output from a circuit toggle with each clock pulse (ie doubling its frequency), by connecting  $\overline{Q}$  with  $D$ , in the following manner:



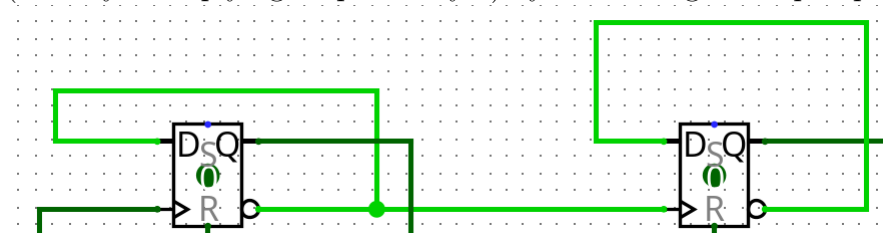Likewise we can make the output from a circuit toggle with every other clock pulse (thereby multiplying its period by 4) by connecting two flip flops in the following manner




Therefore we have the following circuit:

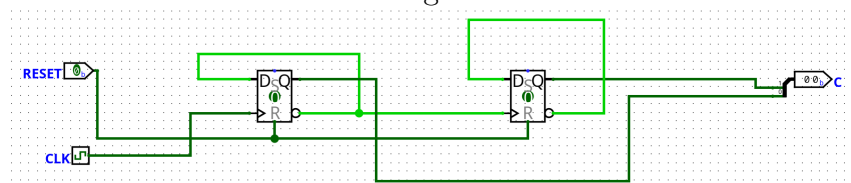
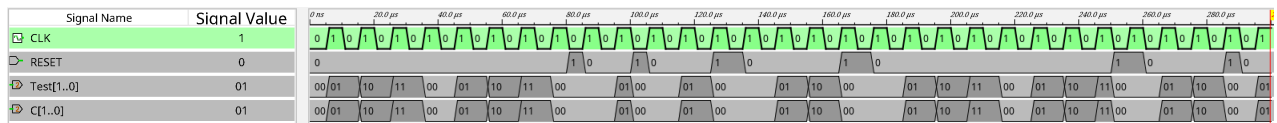
## Problem 5

I created the circuit, and it is shown above, and I tested by comparing its output vs that of a logisim counter, its output is denoted as test in the chronograph below.




As one can see, the chronograph outputs of my counter vs logisim's counter is the same.

## Problem 6

We have the following transition table:

	Prev state	Inputs (REQ,DONE)				OUTPUT	
	$(y_1y_0)^n$	0,0	0,1	1,1	1,0	GO	ACK
S1	0,0	S1			S2	0	0
S2	0,1			S3	S2	1	0
S3	1,1	S4			S3	0	1
S4	1,0	S4	S1			1	1

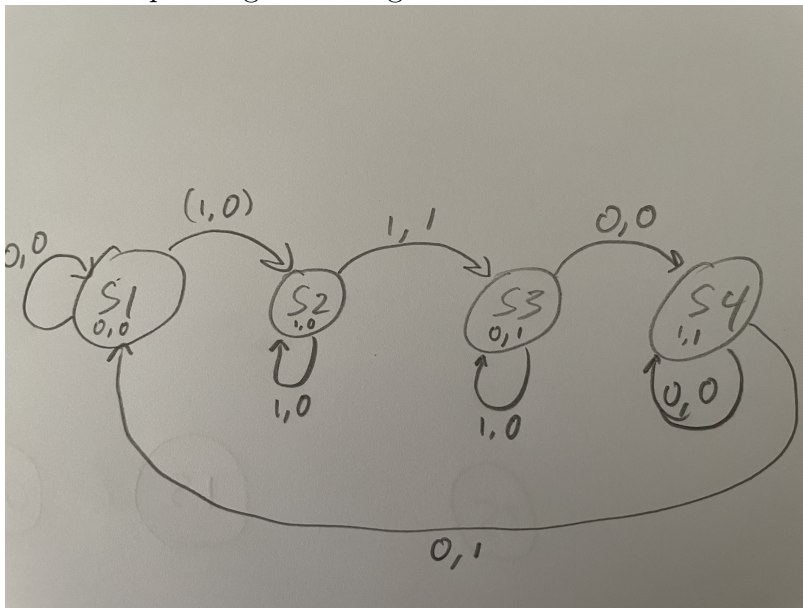The corresponding state diagram is shown below.



And it results in the following kmap for  $y_1$

$y_1, y_0$	Req, Done	
	00	01
00	0	0
01	0	0
11	1	1
10	1	1

Which corresponds with the equation:

$$y_1^{n+1} = y_1^n \cdot \overline{REQ} + DONE \cdot REQ$$

Likewise the kmap for  $y_0$  is shown below.

$y_1, y_0$	Req, Done	
	00	01
00	0	0
01	0	0
11	1	1
10	1	1

Which corresponds with the equation:

$$y_0^{n+1} = y_0^n \cdot REQ + \overline{y_1^n} \cdot REQ$$


We have that

$$GO^{n+1} = y_1^{n+1} \cdot \overline{y_0^{n+1}} + \overline{y_1^{n+1}} \cdot y_0^{n+1}$$


And

$$\begin{aligned} ACK^{n+1} &= y_1^{n+1} \\ &= y_1^n \cdot \overline{REQ} + DONE \cdot REQ \end{aligned}$$

## Problem 7

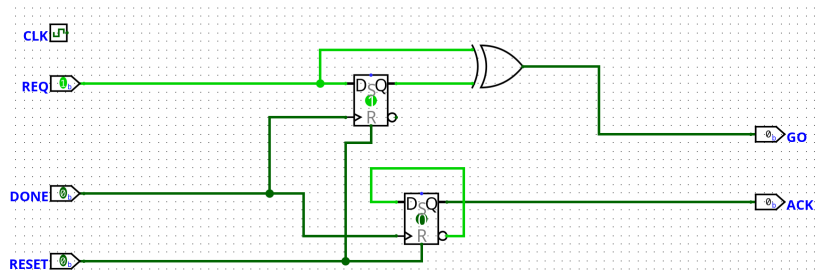


And has a chronograph of:

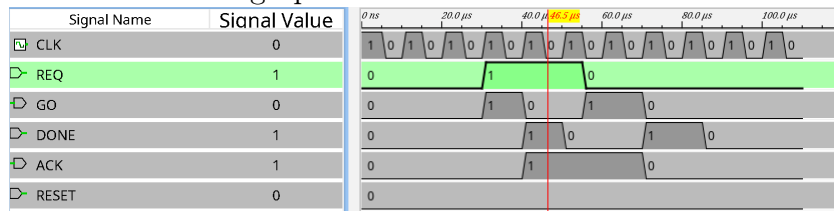

## Problem 8

Using the following flow chart

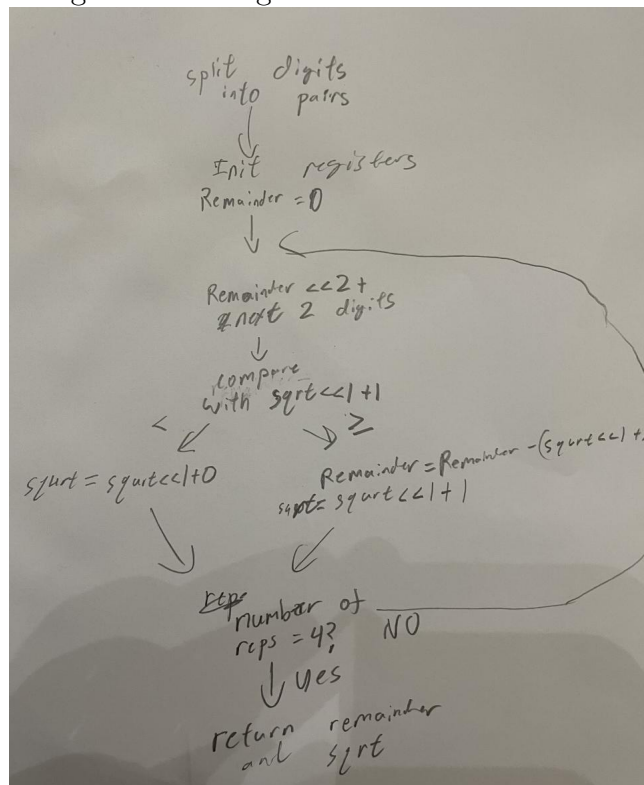

I created the circuit

