

# ECE M16 Final

Lawrence Liu

August 10, 2022

## Problem 1

	1	1	0	1
1	11	00	00	10
	1			
101	10	00		
	1	01		
1100	11	00		
	0			
	11	00	10	
11001	1	10	01	
	1	10	01	


## Problem 2

Basing on the assumption that  $c[1 : 0] = 11$  corresponds with  $o[1 : 0] = i[1 : 0]$  we have that

$$\begin{aligned} a[1] &= \overline{c[1]}. \overline{c[0]}. i[7] + \overline{c[1]}. c[0]. i[5] + c[1]. \overline{c[0]}. i[3] + c[1]. c[0]. i[1] \\ &= \overline{c[1]}. (\overline{c[0]}. i[7] + c[0]. i[5]) + c[1]. (\overline{c[0]}. i[3] + c[0]. i[1]) \end{aligned}$$

$$\begin{aligned} a[0] &= \overline{c[1]}. \overline{c[0]}. i[6] + \overline{c[1]}. c[0]. i[4] + c[1]. \overline{c[0]}. i[2] + c[1]. c[0]. i[0] \\ &= \overline{c[1]}. (\overline{c[0]}. i[6] + c[0]. i[4]) + c[1]. (\overline{c[0]}. i[2] + c[0]. i[0]) \end{aligned}$$

Which results in a circuit like this

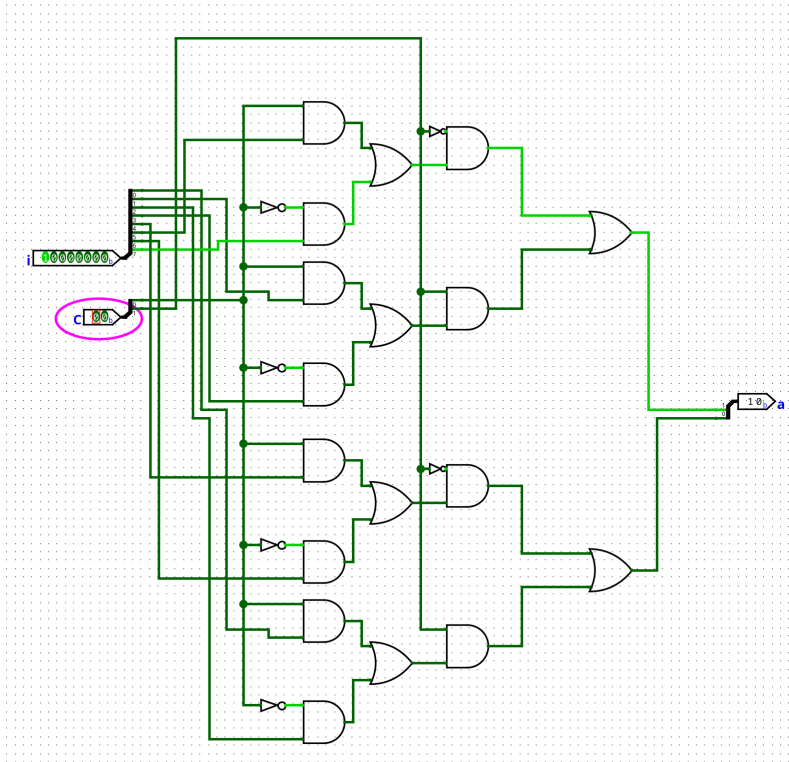

## Problem 3

I created the circuit, and it is shown above, and I tested it with the following python checker script

```

1 import numpy as np
2 import pandas as pd
3 import os
4 from calendar import monthrange
5
6 def RunCircuit(logisim_jar : str, circuit : str):
7     """
8     This function runs the logisim simulator and returns the output of
9     the circuit as
10    a pandas dataframe.
11    """
12    output=os.popen(f"java -jar {logisim_jar} {circuit} -tty table").
13    read()
14    output=[o.split() for o in output.split("\n")[:-1]]
15    return pd.DataFrame(output[1:], columns=output[0])
16
17 def checkQ2(truth_table:pd.DataFrame)->bool:
18     """
19     This function checks the output of the circuit for the truth table
20     and returns
21     weather the output is correct or not.

```

```

19     """
20     #convert hex to binary
21     truth_table['i']=truth_table['i'].apply(lambda x: f'{int(x,16):0>8b}'
22     ')
23     for i,row in truth_table.iterrows():
24         c=int(row.C,2)
25         i=row.i
26         a=row.a
27         #calculate a expected
28         a_expected=i[c*2:c*2+2]
29         #check if a is equal to a_expected
30         if a!=a_expected:
31             print("error!")
32             print(f"at c={row.C}")
33             print(f"expected a={a_expected}")
34             print(f"got a={a}")
35             print(f"i={row.i}")
36             return False
37         return True
38
39 if __name__=="__main__":
40     truth_table=RunCircuit("../logisim-evolution.jar","Logisim/FinalQ3.
41     circ")
42     if checkQ2(truth_table):
43         print("Q2 passed!")

```

This script utilizes Logisim's command line ability. I had the files in the following format

ECEM16

```

|- .gitignore
|- Final
| |- Logisim
| | |- FinalQ3.circ
| :
| :
| |- checker.py
|- .gitignore
|- logisim-evolution.jar

```

## Problem 4

Let the output